Hex rotary switch test - wiring

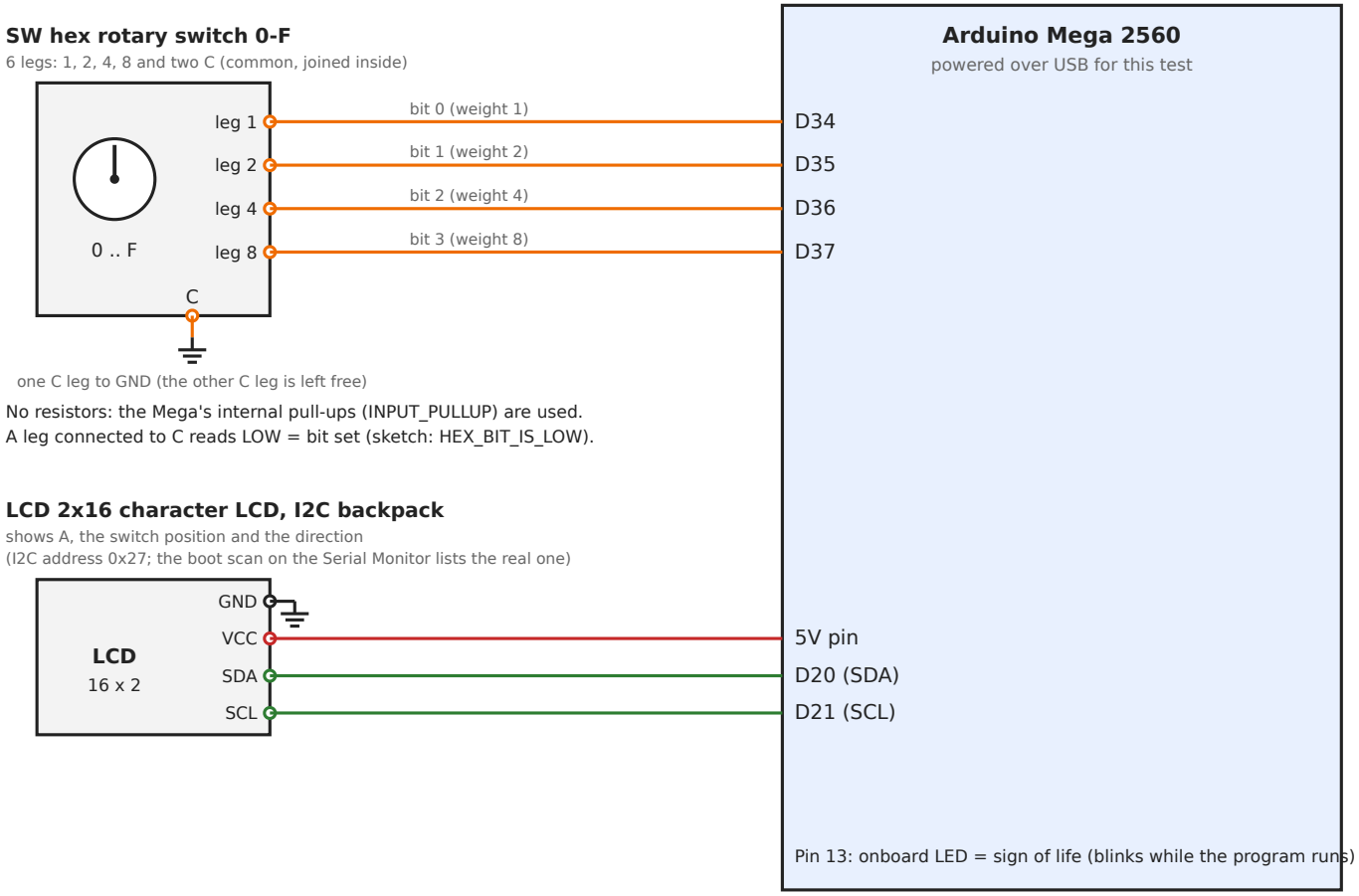

Connections

1. Switch leg 1 -> D34, leg 2 -> D35, leg 4 -> D36, leg 8 -> D37; one C leg -> GND (any Mega GND pin).
2. LCD: GND -> GND, VCC -> 5V, SDA -> D20, SCL -> D21 (the Mega's own I2C pins; no pull-up resistors needed).
3. Power: USB cable to the PC (upload, Serial Monitor at 115200 baud). No LED strips or sticks are connected.
4. If the legs are not marked, look for the numbers 1, 2, 4, 8 and the two letters C on the switch body.
5. If A goes the wrong way: set reverseDirection to true in sketch.ino. If position 0 shows as F: set HEX_BIT_IS_LOW to false (the switch is complement-coded).
6. If the LCD shows no text but its light is on: turn the blue contrast trimmer on the I2C backpack, and check that the LCD VCC pin measures at least 4.75 V (see README.txt).